 


# Memory Systems

Computer Architectures M



# Frequencies vs. periods

1 Hz	1 KHz	1 MHz	1 GHz	1 THz
1000 msec	1000 microsec	1000 nsec	1000 Psec	1 psec
1sec	1 msec	1 microsec	1 nsec	
	40 KHz		250 MHz	60 GHz
	25 microsec		4 nsec	16,6 psec
	25 Hz		3 GHz	
	40 msec		330 psec	



# EPROM memories

## EPROM

1	VPP	VCC	32
2	A16	PGM*	31
3	A15	NC	30
4	A12	A14	29
5	A7	A13	28
6	A6	A8	27
7	A5	A9	26
8	A4	A11	25
9	A3	OE*	24
10	A2	A10	23
11	A1	CE*	22
12	A0	D7	21
13	D0	D6	20
14	D1	D5	19
15	D2	D4	18
16	GND	D3	17

128K × 8

  - Non volatile read-only memories
- Capacities: two's multiples: 32K, 64K, 128K, 256K.....
- Access time: 50-80 ns




# RAM memories(SRAM)

## RAM


1	NC	VCC	32
2	A16	A15	31
3	A14	NC	30
4	A12	WE*	29
5	A7	A13	28
6	A6	A8	27
7	A5	A9	26
8	A4	A11	25
9	A3	OE*	24
10	A2	A10	23
11	A1	CE*	22
12	A0	I/O7	21
13	I/O0	I/O6	20
14	I/O1	I/O5	19
15	I/O2	I/O4	18
16	GND	I/O3	17

128K × 8

## Read Cycle

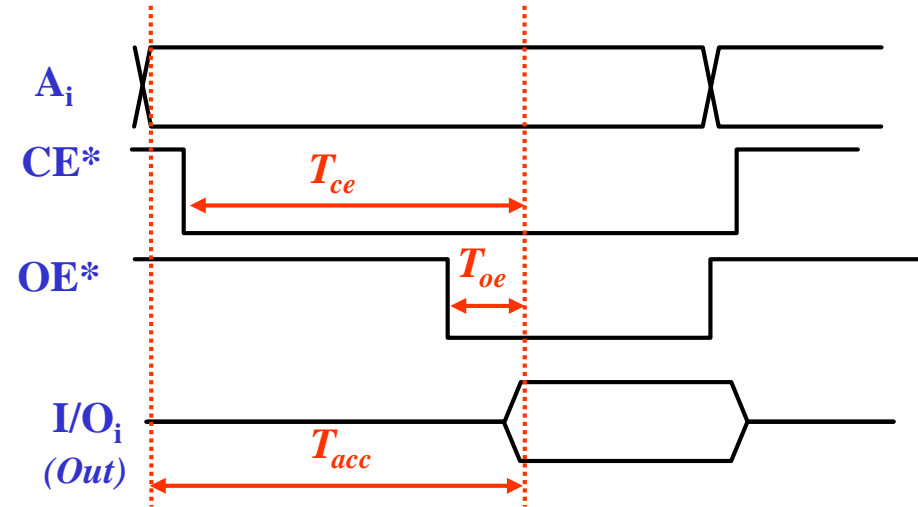

## Write Cycle

 

- Volatiles memories, readable and writable
- Capacity four's multiples: 8K, 32K, 128K, 512K.....
- Access time: 5-40 ns
- DRAM: 1 transistor per bit, higher capacity, less speed

WR RD


Data bit

# RAM cell

D  
E  
C  
O  
D  
E  
R

j

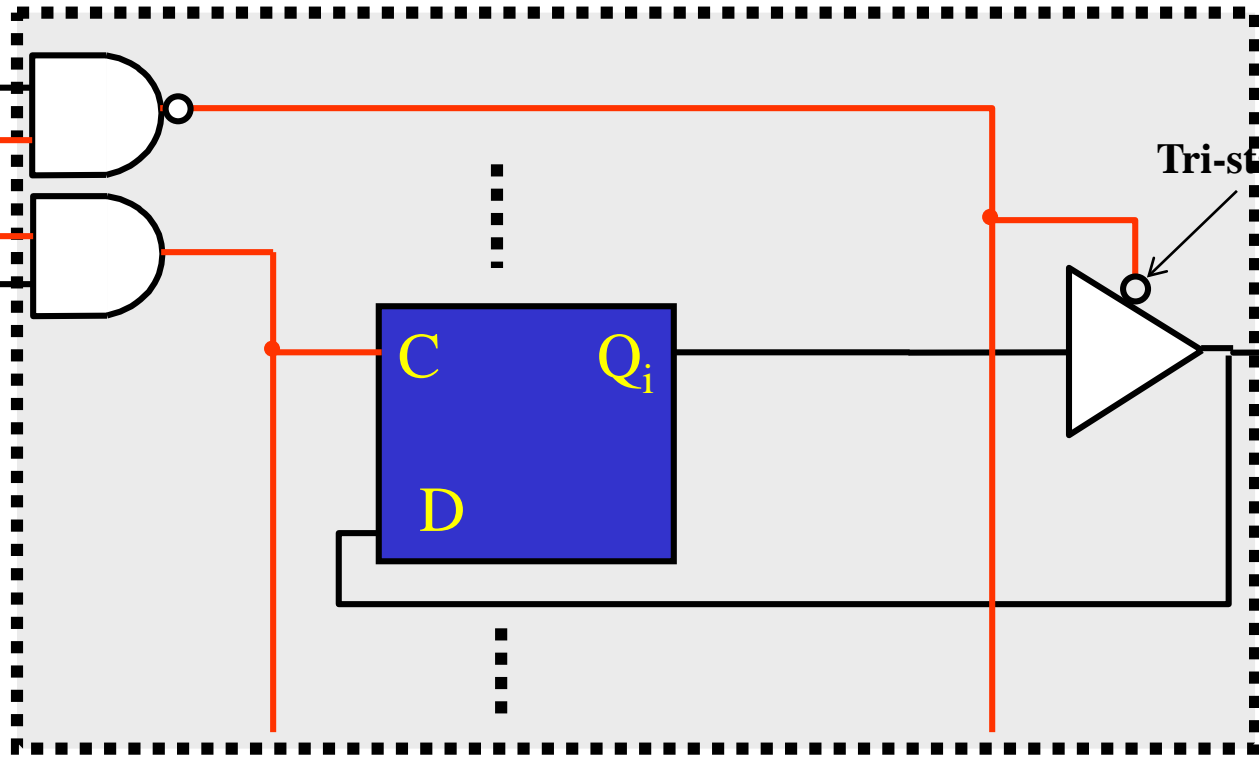$2^n \times N \Rightarrow 2^n$  cells each of N bits




Tri-state driver

Cell Address: "j"

# Decoder and Decoder matrix

(AND => associative property)

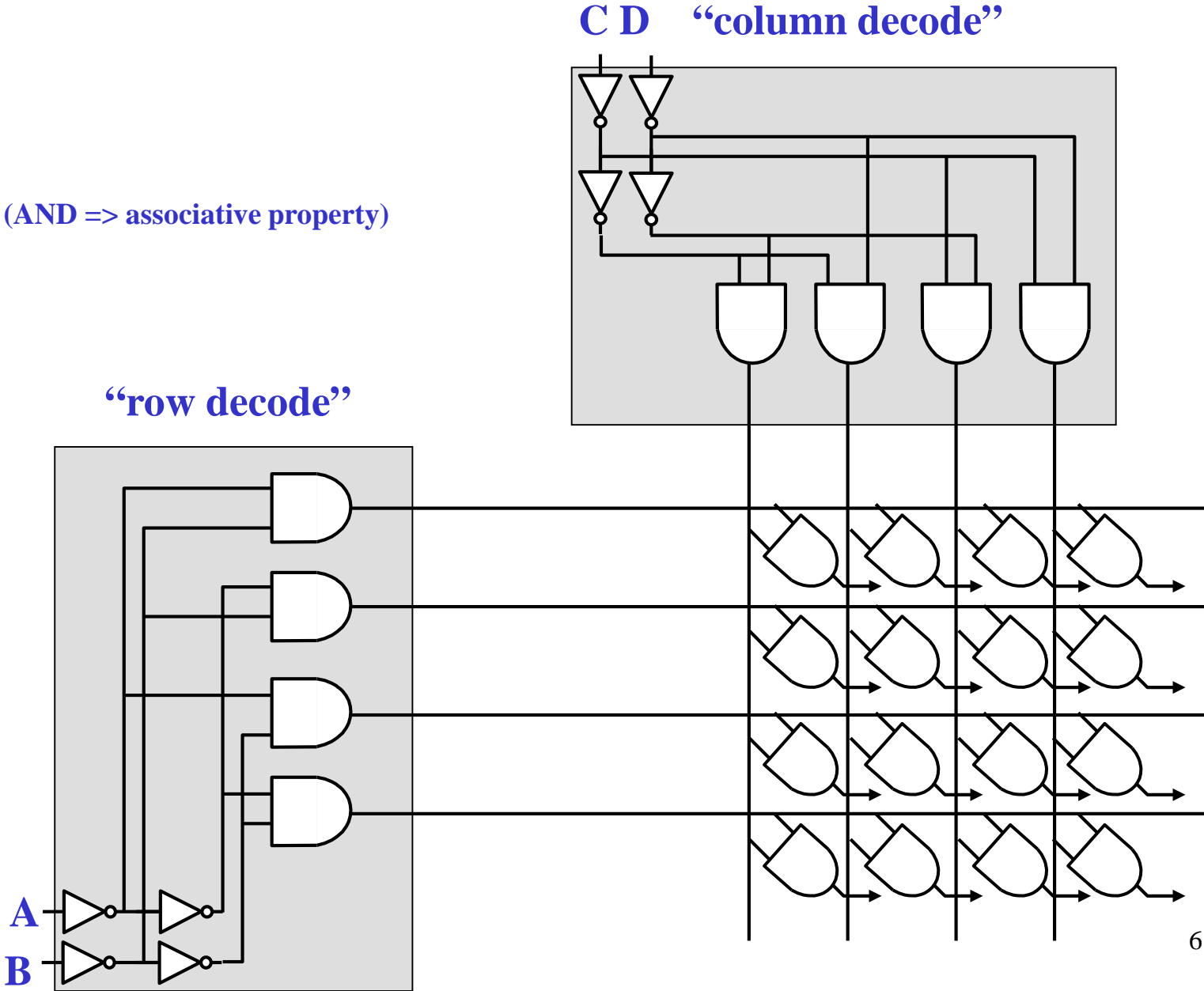


**Pin Configurations**
**Functional Description**


The CY7C199 is a high-performance CMOS static RAM organized as 32,768 words by 8 bits. Easy memory expansion is provided by an active LOW chip enable ( $\overline{CE}$ ) and active LOW output enable ( $\overline{OE}$ ) and three-state drivers. This device has an automatic power-down feature, reducing the power consumption by 81% when deselected. The CY7C199 is in the standard 300-mil-wide DIP, SOJ, and LCC packages.

An active LOW write enable signal ( $\overline{WE}$ ) controls the writing/reading operation of the memory. When  $\overline{CE}$  and  $\overline{WE}$  inputs are both LOW, data on the eight data input/output pins ( $I/O_0$  through  $I/O_7$ ) is written into the memory location addressed by the address present on the address pins ( $A_0$  through  $A_{14}$ ). Reading the device is accomplished by selecting the device and enabling the outputs,  $\overline{CE}$  and  $\overline{OE}$  active LOW, while  $\overline{WE}$  remains inactive or HIGH. Under these conditions, the contents of the location addressed by the information on address pins are present on the eight data input/output pins.


The input/output pins remain in a high-impedance state unless the chip is selected, outputs are enabled, and write enable ( $\overline{WE}$ ) is HIGH. A die coat is used to improve alpha immunity.

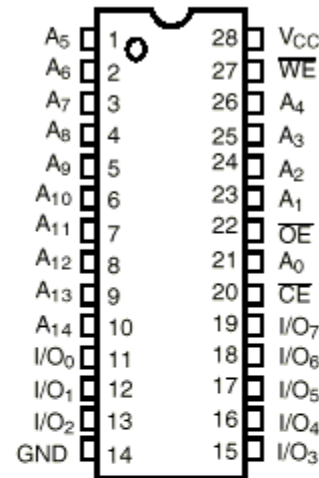**DIP / SOJ / SOIC  
Top View**

  
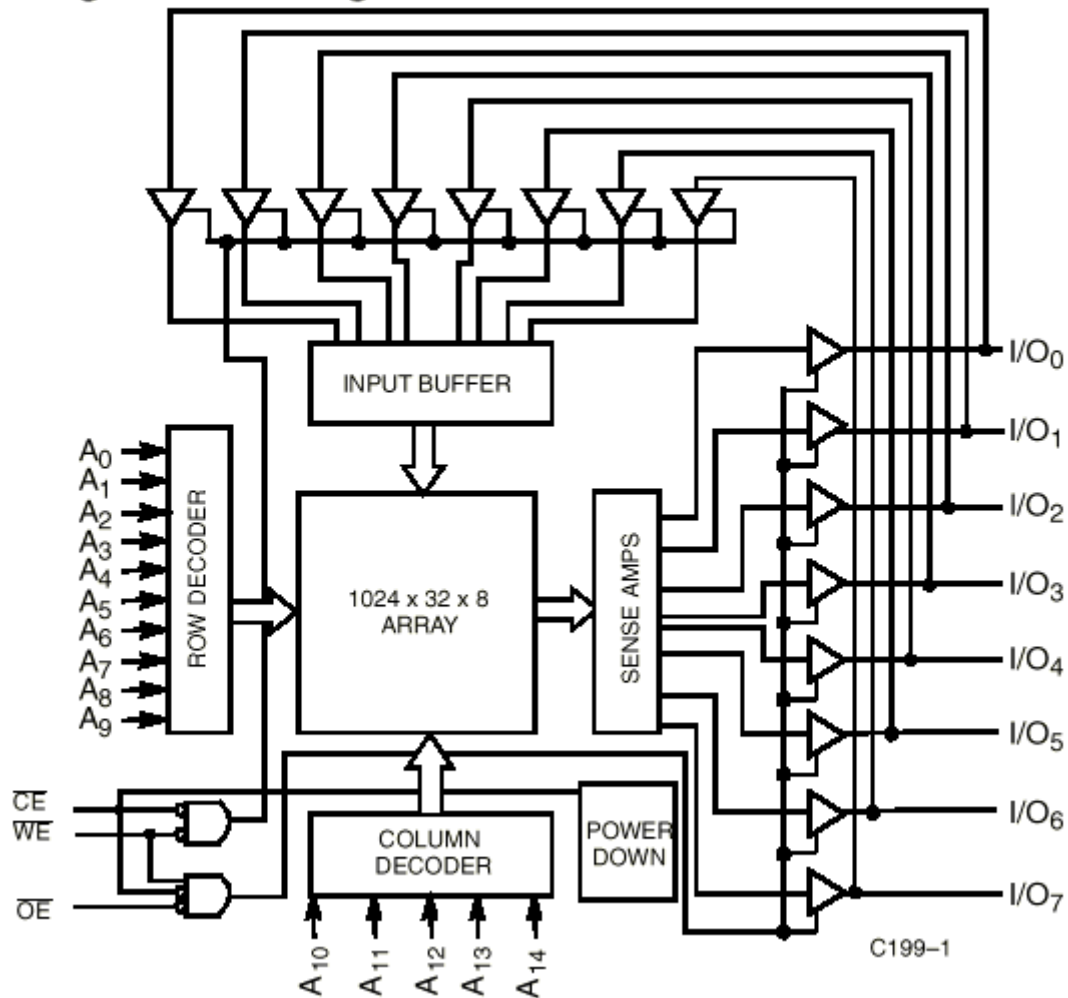
C199-2

**LCC  
Top View**


C199-3


**TSOP I  
Top View  
(not to scale)**

Logic Block Diagram




C199-1






Read Cycle No. 1 [12, 13]

 


Read Cycle No. 2 [13, 14]

 



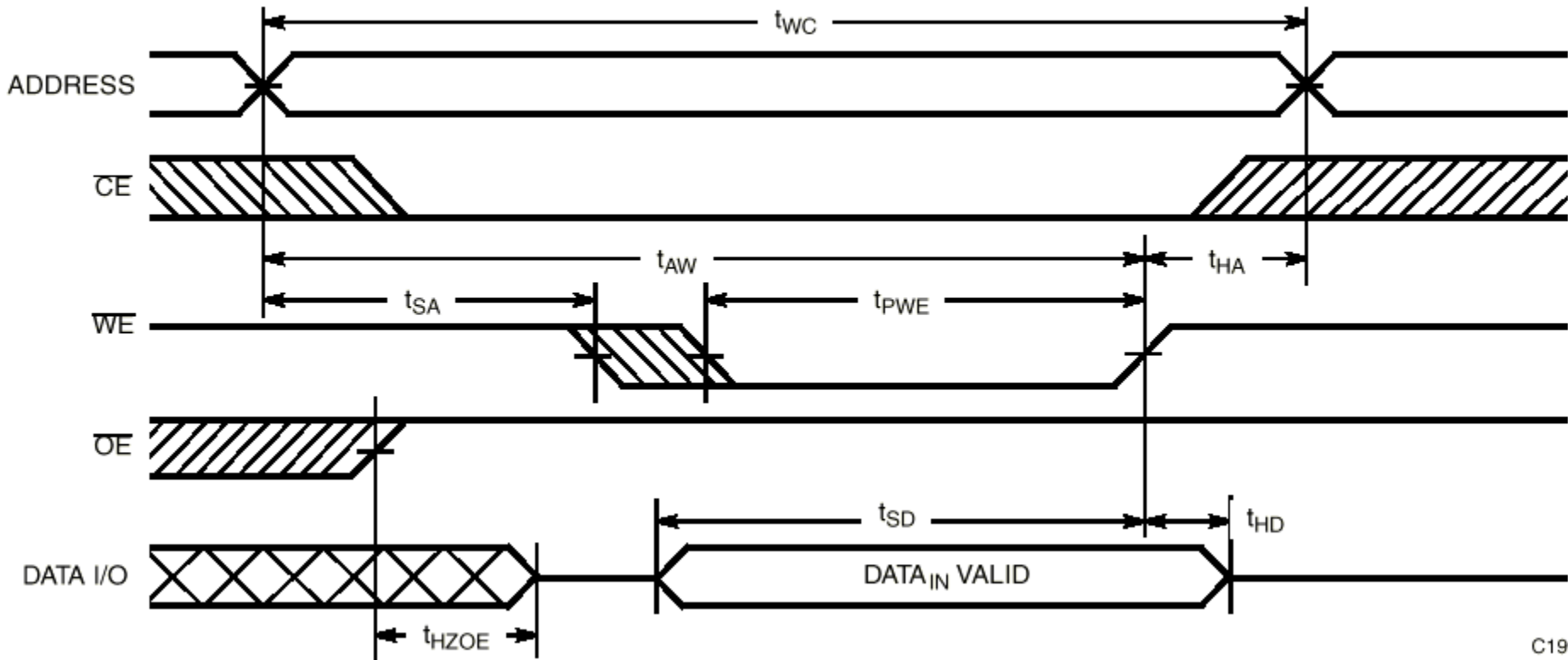
Write Cycle No. 1 (WE Controlled)<sup>[10, 15, 16]</sup>



**Switching Characteristics** Over the Operating Range<sup>[3,7]</sup> (continued)

Parameter	Description	7C199-20		7C199-25		7C199-35		7C199-45		Unit
		Min.	Max.	Min.	Max.	Min.	Max.	Min.	Max.	
<b>READ CYCLE</b>										
t <sub>RC</sub>	Read Cycle Time	20		25		35		45		ns
t <sub>AA</sub>	Address to Data Valid		20		25		35		45	ns
t <sub>OHA</sub>	Data Hold from Address Change	3		3		3		3		ns
t <sub>ACE</sub>	$\overline{CE}$ LOW to Data Valid		20		25		35		45	ns
t <sub>DOE</sub>	$\overline{OE}$ LOW to Data Valid		9		10		16		16	ns
t <sub>LZOE</sub>	$\overline{OE}$ LOW to Low Z <sup>[8]</sup>	0		0		0		0		ns
t <sub>HZOE</sub>	$\overline{OE}$ HIGH to High Z <sup>[8,9]</sup>		9		11		15		15	ns
t <sub>LZCE</sub>	$\overline{CE}$ LOW to Low Z <sup>[8]</sup>	3		3		3		3		ns
t <sub>HZCE</sub>	$\overline{CE}$ HIGH to High Z <sup>[8,9]</sup>		9		11		15		15	ns
t <sub>PU</sub>	$\overline{CE}$ LOW to Power-Up	0		0		0		0		ns
t <sub>PD</sub>	$\overline{CE}$ HIGH to Power-Down		20		20		20		25	ns
<b>WRITE CYCLE</b> <sup>[10,11]</sup>										
t <sub>WC</sub>	Write Cycle Time	20		25		35		45		ns
t <sub>SCE</sub>	$\overline{CE}$ LOW to Write End	15		18		22		22		ns
t <sub>AW</sub>	Address Set-Up to Write End	15		20		30		40		ns
t <sub>HA</sub>	Address Hold from Write End	0		0		0		0		ns
t <sub>SA</sub>	Address Set-Up to Write Start	0		0		0		0		ns
t <sub>PWE</sub>	$\overline{WE}$ Pulse Width	15		18		22		22		ns
t <sub>SD</sub>	Data Set-Up to Write End	10		10		15		15		ns
t <sub>HD</sub>	Data Hold from Write End	0		0		0		0		ns
t <sub>HZWE</sub>	$\overline{WE}$ LOW to High Z <sup>[9]</sup>		10		11		15		15	ns
t <sub>LZWE</sub>	$\overline{WE}$ HIGH to Low Z <sup>[8]</sup>	3		3		3		3		ns
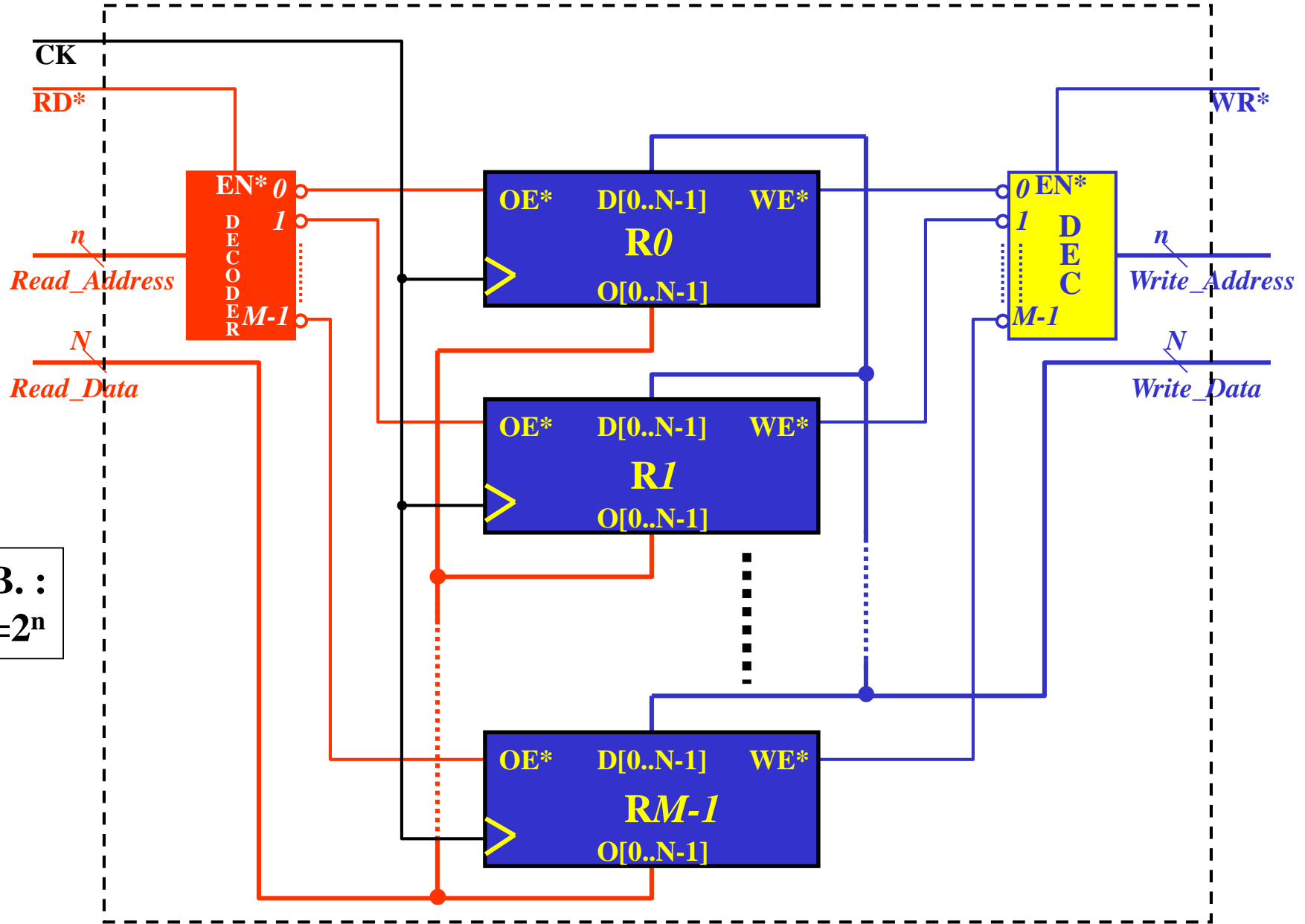
# Register File (1 read-port, 1 write-port)




**N.B. :**  
**M=2<sup>n</sup>**

*A memory device is a register file*
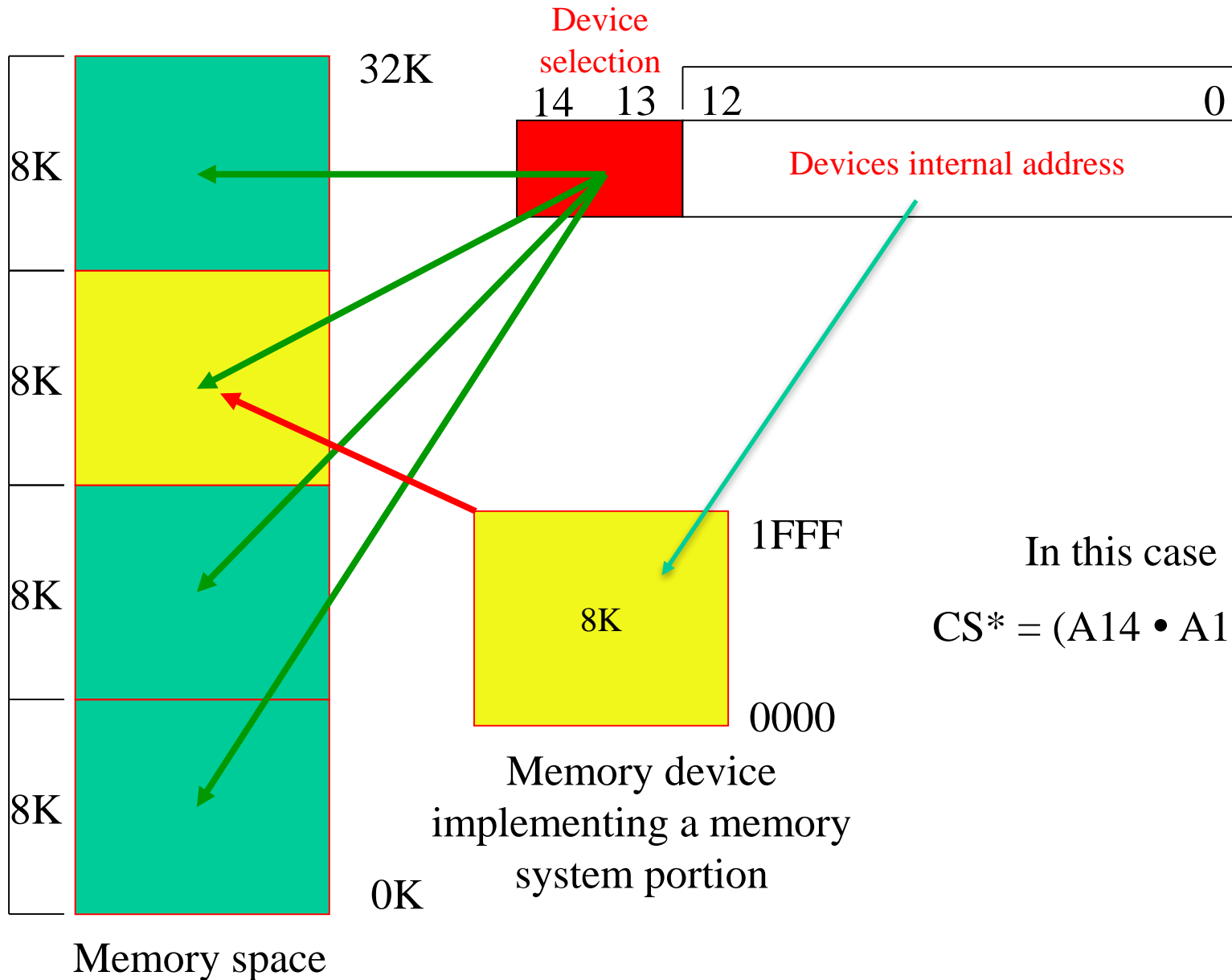
# Memories with $2^k$ bytes


- Any memory (and in particular memories with 8-bit parallelism – the only we will address), with  $2^k$  cells, has internally a **k-variables decoder with E enable (negative true) input** (this means that when  $E = 1$  none of the outputs of the decoder is active) which selects one of the memory bytes. The memory interface has therefore the following signals
- Address bits ( $A_n \dots A_0$ ) which select the addressed byte (if E enabled)
- Data bits ( $D_7 \dots D_0$ )
- At least one *chip select* ( $CS^*$ ) (called also “*chip enable*” ( $CE^*$  - asterisk means «negative true») which is the enable of the decoder. If  $CS^*$  is inactive (=1) it means that no byte of this memory (of this «chip») is addressed.  $CS^*$  is used to selected a memory device when multiple devices are present
- A memory bank (device) is «aligned» if its lowest address **within the entire memory system** is located at an address multiple of  $2^k$  (a 4 cells device is aligned if its two LSBs address are 0 – multiple of 4 -, a 64K cells device if its 16 LSBs are 0 etc.)
- A Read Command ( $RD^*$ ) which enables the data onto the bus. Normally there is also an Output Enable ( $OE^*$ ) signal. The addressed byte of the memory is output only if  $CS^*=RD^*=OE^*=0$
- If the memory is a RAM (read/write memory) another signal is present: write command  $WR^*$  or  $WE^*$  which allows to store bus data into the selected memory byte. Obviously this can occur only if  $CS^*=RD^*=OE^*=0$
- Needless to say  $RD^*$  and  $WR^*$  are mutually exclusive
- In a system there are normally multiple memory devices in order to implement memory systems bigger than a single device. Multiple devices are therefore needed, each one implementing a portion

An example: a 32 Kbytes memory system made with 8K devices  
 32 Kbytes correspond to a 15 bit address




In this case  
 $CS^* = (A14 \cdot A13^*)^*$

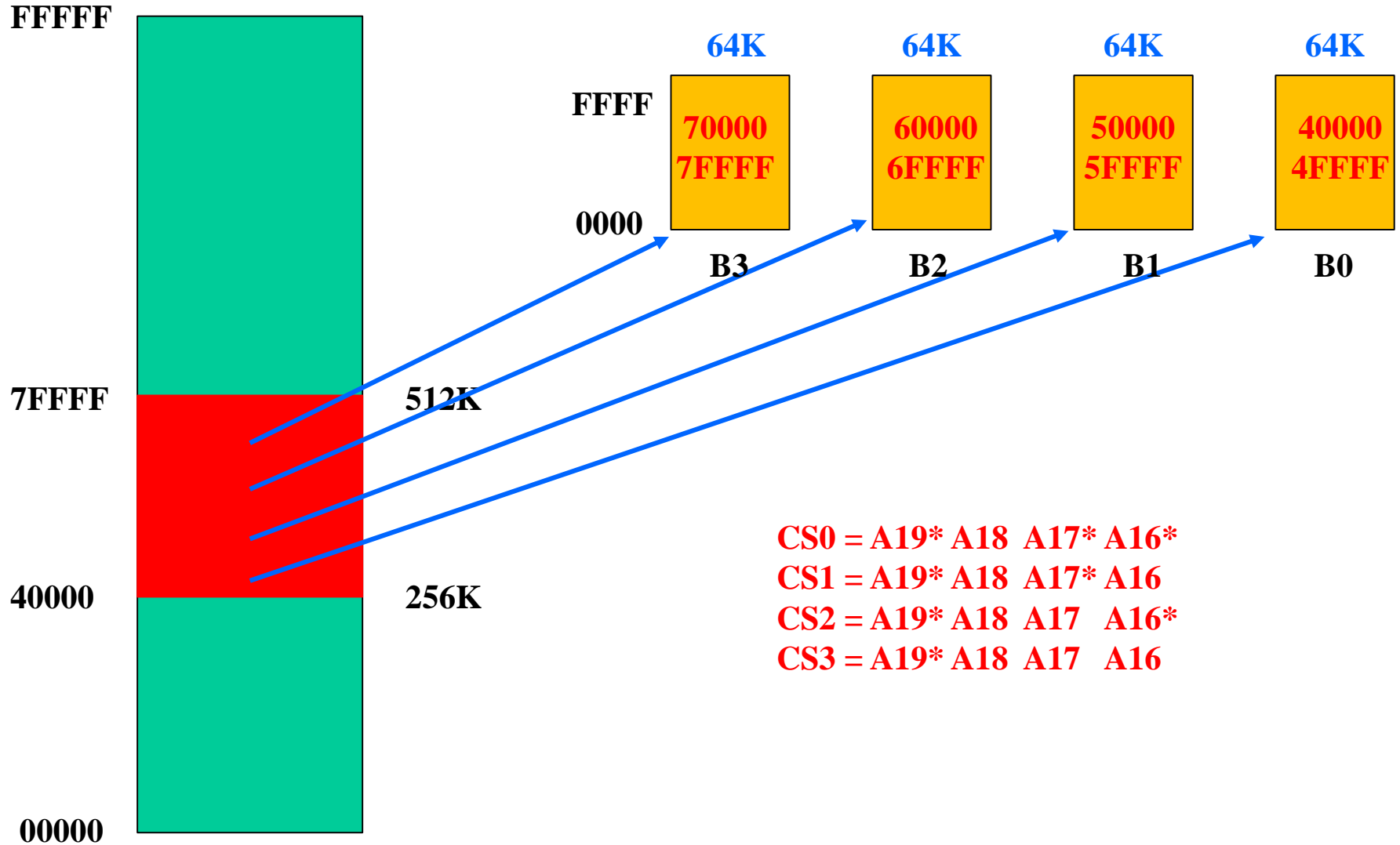1MB address space (20 bit address 0-19) - 8 bit parallelism memory  
 64K bit ROM devices  
 256K memory bank – Addresses 40000-7FFFF



# Memory systems with parallelism > 8

## An example: a 16 bit bus

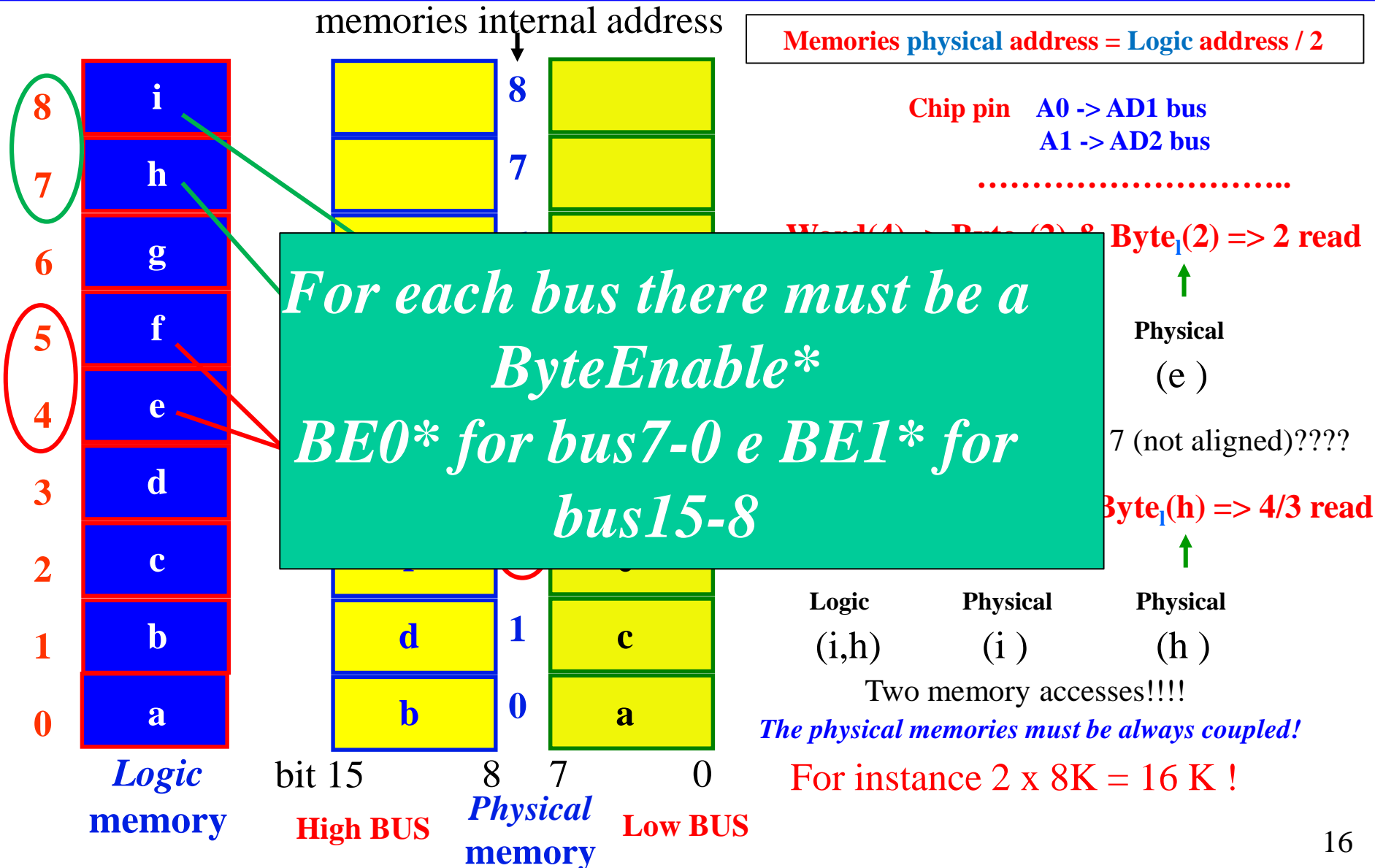



## Memory systems with parallelism > 8

### An example: a 16 bit bus

`mov al, even_byte_address ;` transfer one byte at even address => one bus cycle 8 bit => BE0\*

`mov al, odd_byte_address ;` transfer one byte at odd address => one bus cycle 8 bit => BE1\*


`mov ax, even_word_address ;` transfer one word at even address => one bus cycle 16 bit => BE0\* and BE1\*

`mov ax, odd_word_address ;` transfer one word at odd address => **two** 8 bit cycles => BE1\* and then BE0\*

## MEMORIES in a 16 BIT SYSTEM (I.E. 8086)

The routing of byte high *external* to byte low *internal* is implemented within the microprocessor chip

BE1*	BE0*	
0	0	Word
0	1	High Byte (odd addr.)
1	0	Low Byte (even addr.)
1	1	No transfer

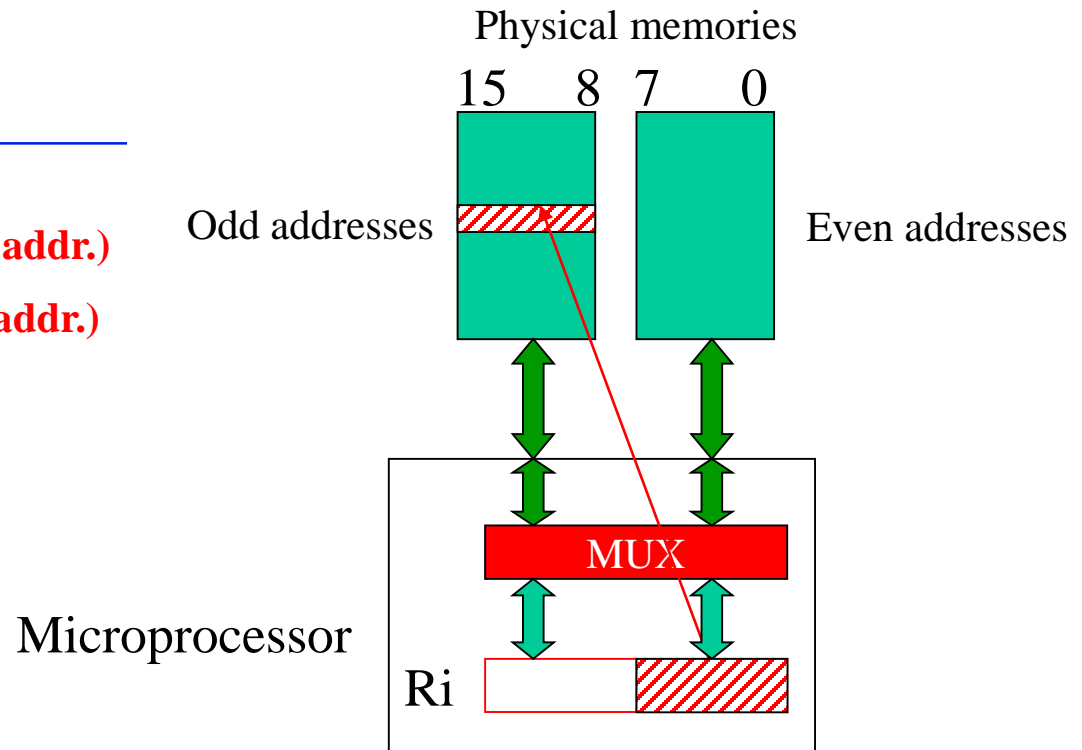

**A0** of the processor *not* generated (instead BE0\* and BE1\*)


**A1** of the processor connected to chip pin A0

**A2** of the processor connected to chip pin A1

*etc. etc.*

# Memory systems with parallelism > 8
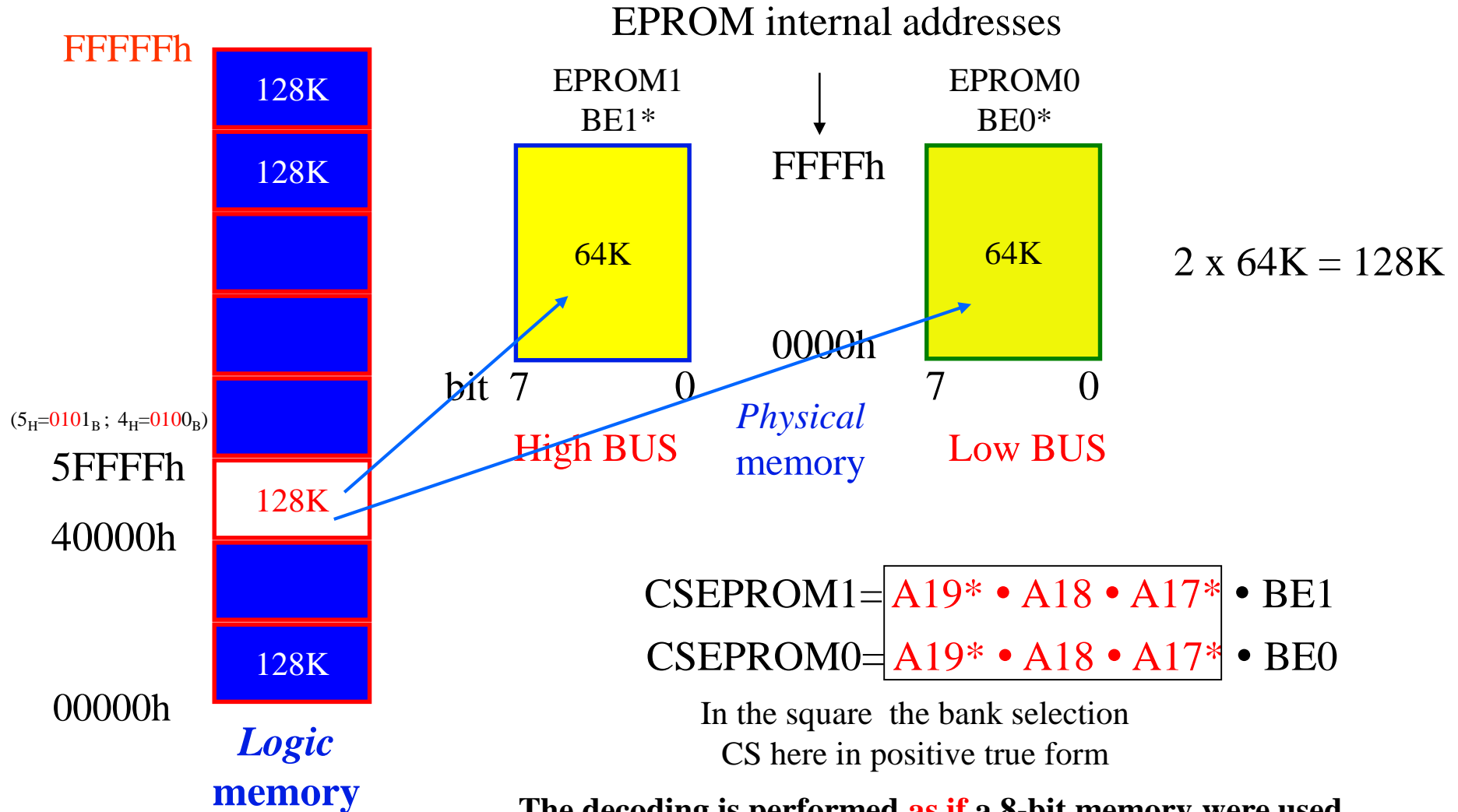
## A 16 bit bus in a 1MB memory (19 to 0 addresses)




The decoding is performed **as if** a 8-bit memory were used.  
 Devices (a couple!) (each one half size of the bank) are used  
 and selected by BE0 e BE1

**Memory systems with parallelism > 8**  
**A 16 bit bus in a 1MB memory (19 to 0 addresses)**


EPROM internal addresses

Logic Memory

EPROM internal addresses

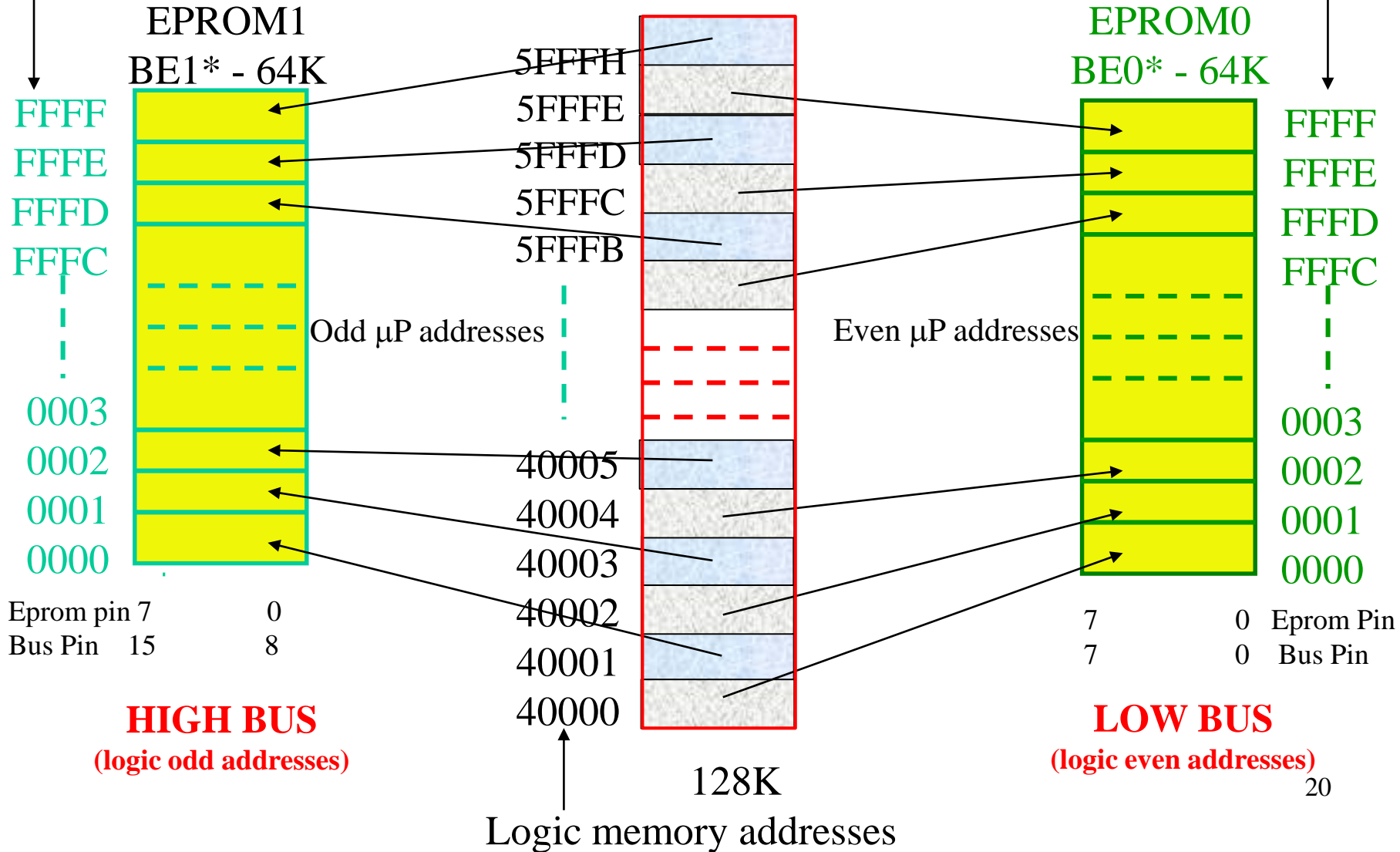

**Memory systems with parallelism > 8**  
**A 32 bit bus**

 

**Always 4**  
**coupled devices**  
 -----  
**Internal memories**  
**physical address is the**  
**processor address/4**

## 32 BIT bus memories

BE3*	BE2*	BE1*	BE0*	
0	0	0	0	Word 32 bit
1	1	0	0	Half word low
0	0	1	1	Half word high
1	1	1	0	byte 0-7
1	1	0	1	byte 15-8

.....

*etc.*

***N.B. Processor A0 and A1 are not generated  
(instead BE0\*, BE1\*, BE2\*, BE3\* are generated)***


***Processor A2 connected to memories A0***

***Processor A3 connected to memories A1***


***etc. etc.***
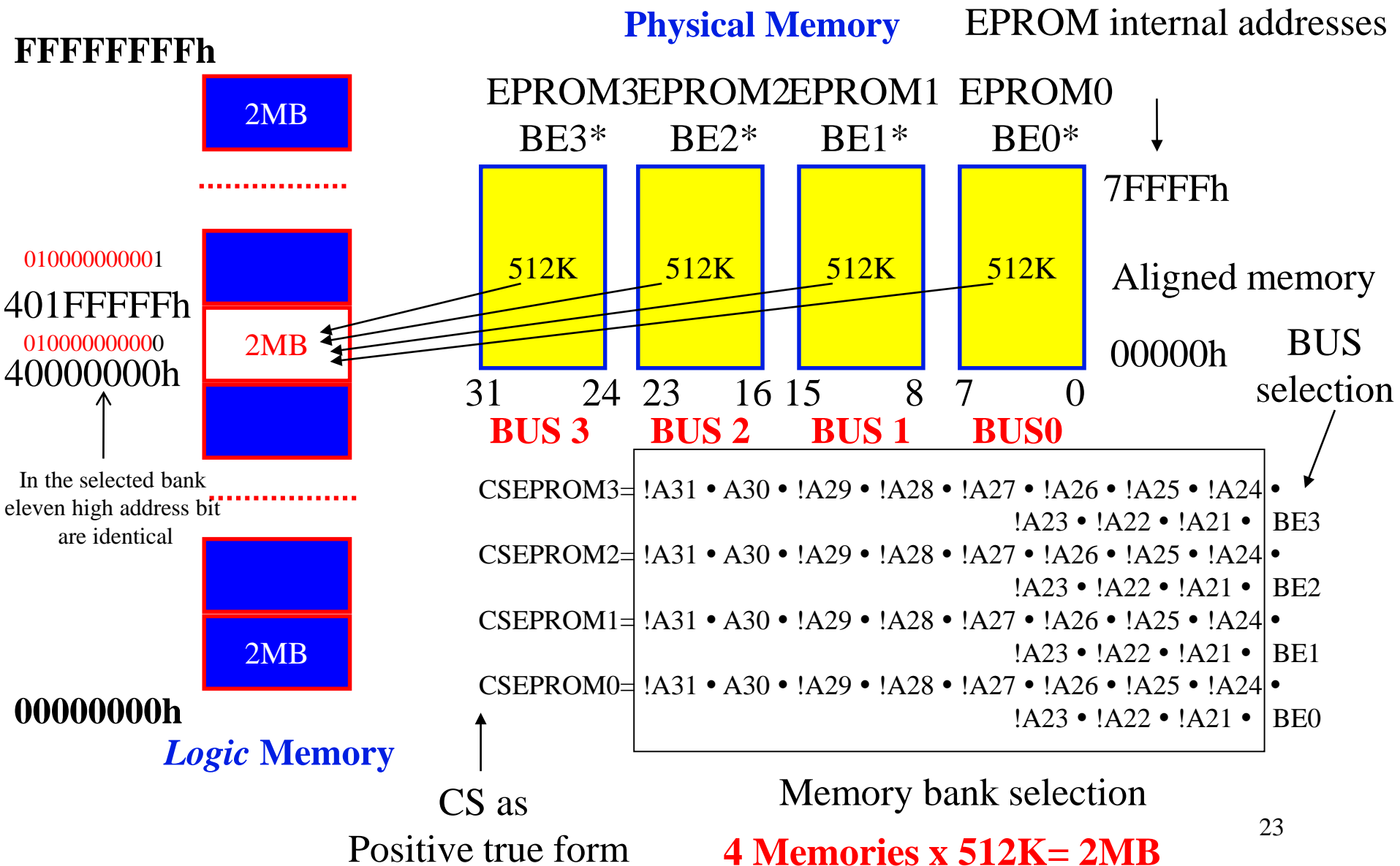
# 32 BIT bus memories

(NB the symbol ! before a logic variable is equivalent to asterisk and means **negation**)




# 32 BIT bus memories

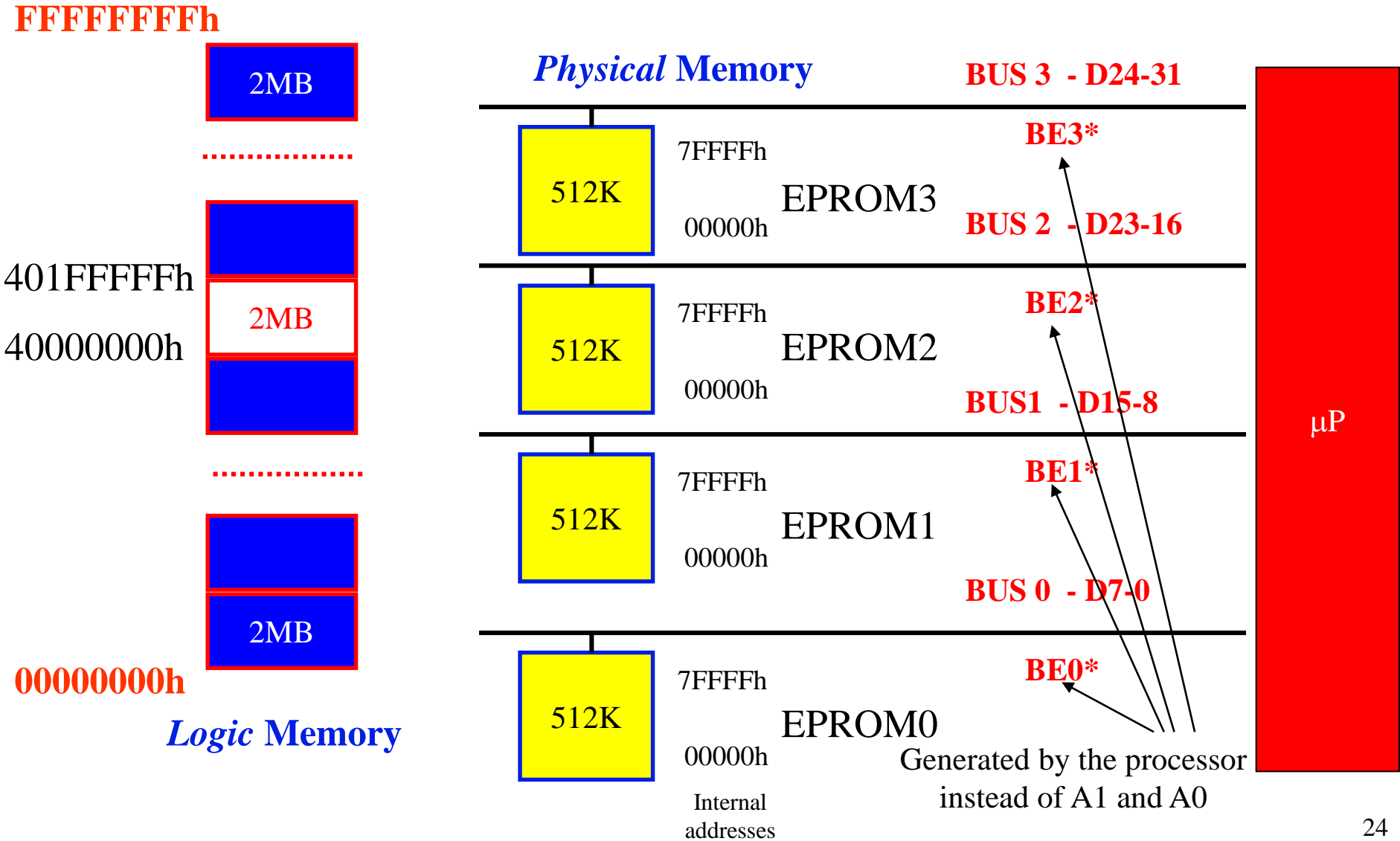



# 32 BIT bus memories

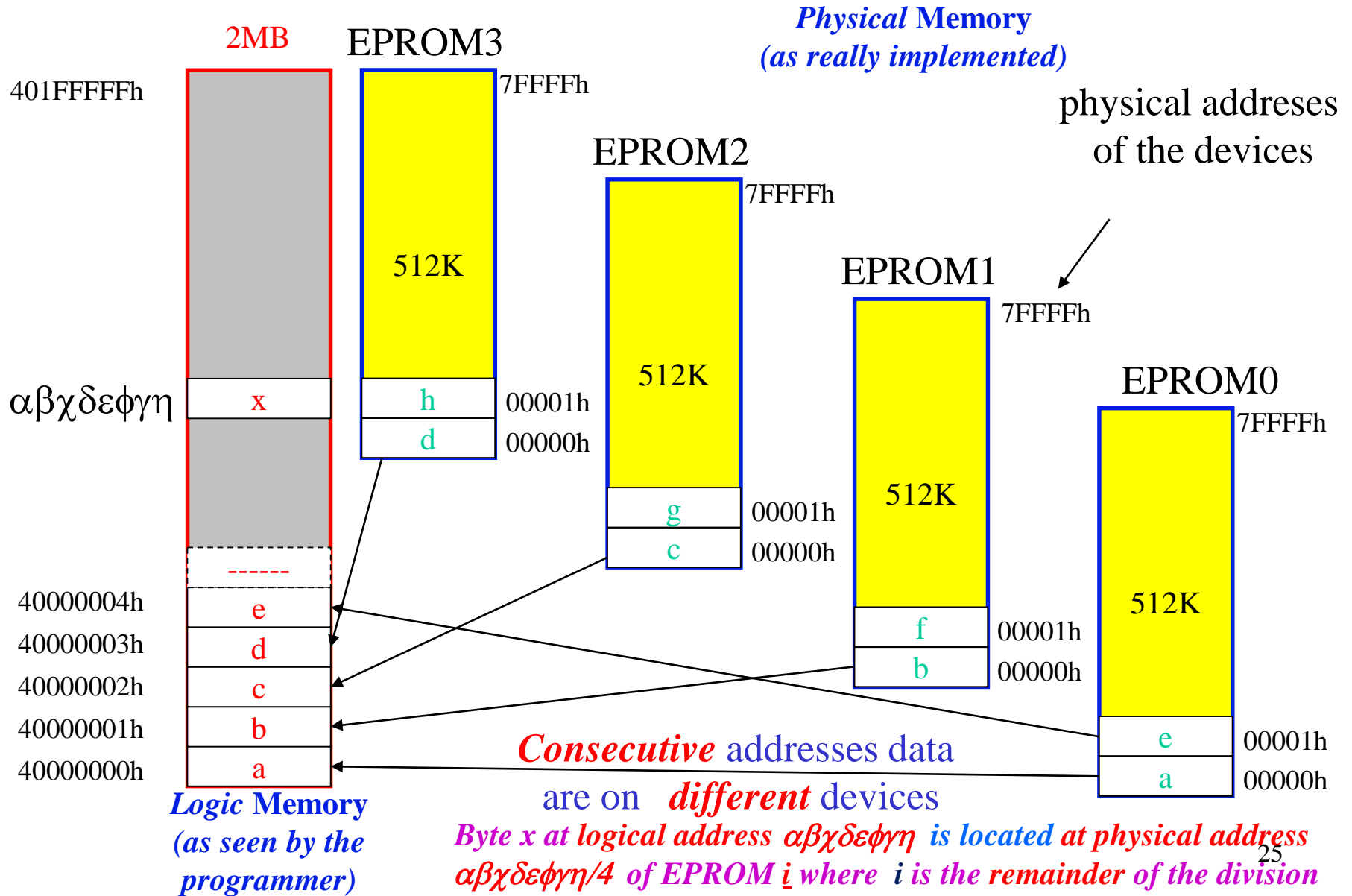

## Exercise

A 256K memory RAM (32 bit parallelism) bank starting at address 84000000H in a 4GB memory space using the minimum number of devices.

What if the parallelism were 64 bit?

## Exercise

A 256K memory RAM (32 bit parallelism) starting at address 84000000 (aligned) in a 4GB memory space .

Address range 84000000-8403FFFF. Devices: 8X32 K RAM devices (**64K RAM do not exist!!!!**)

Therefore two banks of 128K : the first implements the range 84000000 to 8401FFFF and the other the range 84020000 to 8403FFFF. The 32K memory chips use internally the addresses A14-A0 which are connected to bus addresses BA16-BA2 . Notice that bus address BA17 separates the two banks

### *First bank*

CSRAM00=(BA31•BA30!•BA29!•BA28!•BA27!•BA26 •...•BA18!**BA17!**)•BE0

CSRAM01=(BA31•BA30!•BA29!•BA28!•BA27!•BA26 •...•BA18!**BA17!**)•BE1

CSRAM02=(BA31•BA30!•BA29!•BA28!•BA27!•BA26 •...•BA18!**BA17!**)•BE2

CSRAM03=(BA31•BA30!•BA29!•BA28!•BA27!•BA26 •...•BA18!**BA17!**)•BE3

### *Second bank*

CSRAM10=(BA31•BA30!•BA29!•BA28!•BA27!•BA26 •...•BA18!**BA17**) •BE0

CSRAM11=(BA31•BA30!•BA29!•BA28!•BA27!•BA26 •...•BA18!**BA17**) •BE1

CSRAM12=(BA31•BA30!•BA29!•BA28!•BA27!•BA26 •...•BA18!**BA17**) •BE2

CSRAM13=(BA31•BA30!•BA29!•BA28!•BA27!•BA26 •...•BA18!**BA17**) •BE3

If the parallelism of the memory were 64 bit the 8 CS (CSRAM00..CSRAM07) would **NOT** be affected by BA17: **BE7-BE0** instead would play its role. The 8 devices would implement the entire memory bank and memory chips addresses A14-A0 would be connected to **bus addresses BA17-BA3** !! *It is the parallelism which changes not the address range!!!*